

THE KAVERY ENGINEERING COLLEGE
(An Autonomous Institution)

**B.E/B.TECH DEGREE END SEMESTER THEORY EXAMINATIONS, APRIL-MAY
2025**

Fifth Semester

Electrical and Electronics Engineering

EE3501 – Power System Analysis

Regulations - 2021

Duration : 3 Hrs


Maximum : 100 Marks

PART – A (ANSWER ALL QUESTIONS) (Marks 10*2=20)

Q.No	Questions	BLT	CO	Marks
1.	State the need for system analysis in the planning and operation of the power system.	L2	1	2
2.	An alternator rated at 30 MVA, 11 kV has a reactance of 20%. Calculate its p.u. reactance for a base of 50 MVA and 10 kV.	L3	1	2
3.	Compare the Gauss-Seidel method with the Newton-Raphson method.	L4	2	2
4.	Analyze the effects of using a flat voltage start on the convergence speed and accuracy of load flow calculations in power systems.	L4	2	2
5.	A network has a transient reactance of 25% with generator emf equal to 1 p.u. Compute the transient current in the network.	L3	3	2
6.	Draw the oscillation characteristics of a generator when a sudden 3 ϕ short circuit fault occurs at the terminals of an unloaded generator.	L3	3	2
7.	Define unsymmetrical fault and mention its types.	L1	4	2
8.	Draw the sequence network for line-to-line fault in a power system network.	L3	4	2
9.	State equal area criterion.	L1	5	2
10.	Draw the power angle curve of a synchronous machine.	L3	5	2

PART – B (ANSWER ALL QUESTIONS) (Marks 5*16 = 80)

Q.No	Questions	BLT	CO	Marks
11. a i	Obtain the reactance diagram for the figure below using a base of 100 MVA, 220 kV in the j50 Ω line.	L3	1	8

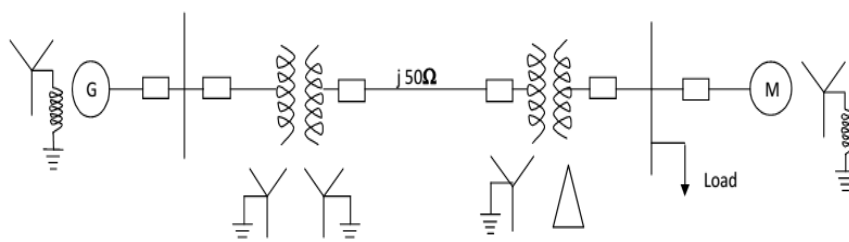

Generator: 40 MVA, 25 kV, $X'' = 20\%$


Synchronous motor: 50 MVA, 11 kV, $X'' = 30\%$

Star – Star transformer: 40 MVA, 33/220 kV, $X = 15\%$

Star – Delta transformer: 30 MVA, 11/220 kV, $X = 15\%$

Load: 11kV, 50 MW + j 68 MVAR

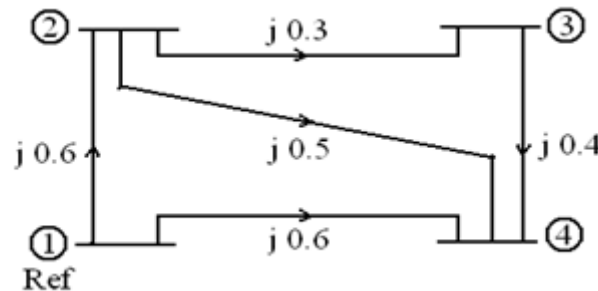- ii Formulate Y_{bus} using the singular transformation method for the network shown in Fig. The impedance is given in p.u. Use node 1 as a reference. L2 1 8



Or

- b i Formulate the bus admittance matrix for a four-bus system data, as given in the table below. L3 1 8

S. No	Line (bus to bus)	Resistance in p.u	Reactance in p.u
1.	1-2	0.05	0.15
2.	1-3	0.10	0.30
3.	2-3	0.15	0.45
4.	2-4	0.10	0.30
5.	3-4	0.05	0.15

- ii Explain the modeling of the Generator and Transformer for the power flow study in detail. L2 1 8

12. a i For a three-bus power system network, obtain the complex bus bar voltage at bus 2 at the end of Gauss-Seidel's first iteration. The line impedance connected between buses 1 and 2 is $(0.04+j0.06)$ p.u and the impedance between buses 2 and 3 is $(0.02+j0.03)$ p.u. Voltage $V_1= 1.0$ p.u. $P_2+jQ_2= (-0.2+j0.5)$, $V_3= 1.02$ p.u. L3 2 8

- ii Explain the steps in the Gauss-Seidel method for power flow analysis and draw a flowchart illustrating each step. L2 2 8

Or

- b i A four-bus system has the following line reactances: L3 2 8

Line code	Reactance in p.u
1-2	j0.5
2-3	j1.0
3-4	j1.0
1-4	j0.5

The bus specifications and values of injected powers are as follows:


Bus	P	Q	V	Bus Specifications
1	-	-	1.05	Slack bus
2	-0.1	0	-	Load bus
3	0.5	-	1.04	Generator bus

4	-0.4	-0.05	-	Load bus
---	------	-------	---	----------

Use the Gauss-Seidel method and find the value of V_2 after the first iteration.

- ii Construct a flowchart for the Newton-Raphson method, detailing each stage of the iterative process in power flow analysis. L1 2 8

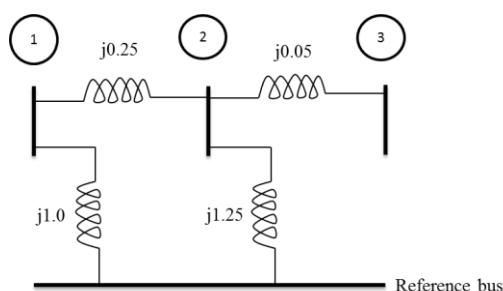13. a i Find the bus impedance matrix for the network shown in the following figure. L3 3 8



- ii Explain the procedure for calculating the fault current and fault MVA of a typical power system network. L2 3 8

Or

- b i The current flowing in the lines toward a balanced load connected in Δ are $I_a = 100 \angle 0^\circ$, $I_b = 141.4 \angle 225^\circ$ and $I_c = 100 \angle 90^\circ$. Find the symmetrical components of the given line currents and draw phasor diagrams of the positive and negative- -sequence line and phase currents. L4 3 8

- ii With the help of a detailed flowchart, explain how a symmetrical fault can be analyzed using Z_{bus} ? L2 3 8

14. a i Derive the necessary equation to determine the fault current for a single line to ground fault for an unloaded generator with its sequence networks. L3 4 8

- ii Draw and explain the sequence impedance networks of transmission lines using symmetrical components. L3 4 8

Or

- b i Derive the fault current for a double line to ground fault for an unloaded generator using symmetrical components. L3 4 10

- ii The positive sequence impedance matrix of a 2-bus system is $j \begin{bmatrix} 0.15 & 0.20 \\ 0.10 & 0.30 \end{bmatrix}$ p.u. Find the fault current when the symmetrical fault occurs at bus 2. L3 4 6

15. a i Derive the power angle equation of a two-machine system. L3 5 8

- ii Derive the expression for equal area criterion for a single machine connected to an infinite bus system. L3 5 8

Or

- | | | | | |
|-----|---|----|---|---|
| b i | Solve the swing equation using modified Euler's method in the study of power system. | L3 | 5 | 8 |
| ii | A 50 Hz, 4 pole alternator rated 100 MVA, 11 kV has an inertia constant of 5 MJ / MVA. (i) Determine the stored energy in the rotor at synchronous speed (ii) Calculate rotor acceleration for $P_m=60$ MW and $P_e=40$ MW. | L3 | 5 | 8 |