

THE KAVERY ENGINEERING COLLEGE
(An Autonomous Institution)

BE/B.TECH DEGREE END SEMESTER THEORY EXAMINATIONS, NOV /DEC 2024

Fifth Semester

Electrical and Electronics Engineering

EE3501 – POWER SYSTEM ANALYSIS

Regulations - 2021

Duration : 3 Hrs


Maximum : 100 Marks

PART – A(ANSWER ALL QUESTIONS) (Marks 10*2=20)

Q.No	Questions	BLT	CO	Marks
1.	What is pu? State its advantages.	RE	1	2
2.	Illustrate the new p.u. impedance if the new base MVA is twice the old base MVA.	UN	1	2
3.	Classify the busses with their known and unknown quantities.	RE	2	2
4.	Relate the necessity of swing bus or slack bus in power system.	UN	2	2
5.	What is solid fault or bolted fault?	RE	3	2
6.	Define fault MVA.	RE	3	2
7.	Draw the sequence network of Δ - Δ connected transformer.	UN	4	2
8.	What are the symmetrical components of a three-phase system?	RE	4	2
9.	Define transient stability of a power system.	RE	5	2
10.	State equal area criterion.	RE	5	2

PART – B (ANSWER ALL QUESTIONS) (Marks 5*13 = 65)

Q.No	Questions	BLT	CO	Marks
11. a	Draw the per unit reactance diagram for the power system shown below. Neglect resistance and use a base of 100 MVA, 220kV in 50 ohms line. The ratings of the generator, motor and transformer are: G: 40MVA, 25kV, $X''=20\%$, M: 50MVA, 11kV, $X'=30\%$, YY Transformer: 40MVA, 33Y/220Y kV, $X=15\%$, Y Δ Transformer: 30MVA, 11 Δ /220Y kV, $X=15\%$, Load:11kV,50MW+j68MVAR	AP	1	13

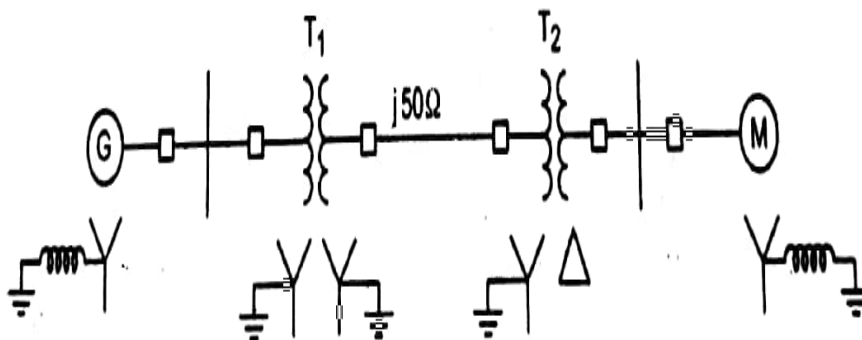

Or

- b Form Y_{bus} by singular transformation method. AP 1 13

S. No.	Self		Mutual	
	Bus code	Impedance	Bus code	Impedance
1	1 – 2	0.5	1 – 2	0.1
2	1 – 3	0.6		
3	3 – 4	0.4		
4	2 – 4	0.3		

12. a Explain the step by step algorithm for load flow solution including voltage controlled buses using Gauss Seidel method. UN 2 13

Or


- b Explain the step by step algorithm for load flow solution using Newton Raphson method. UN 2 13

13. a i Describe the approximations in short circuit analysis. UN 3 4

- ii Explain the short circuit analysis using Thevenin's theorem. UN 3 9

Or

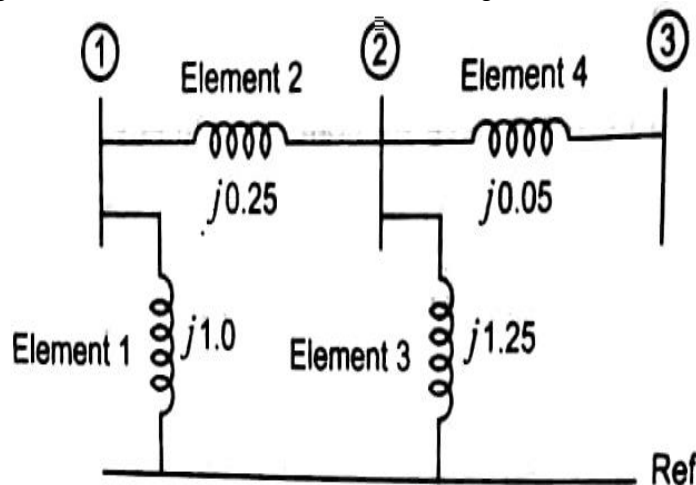- b Determine Z_{bus} using bus building algorithm by adding the lines as per increasing element number. The reactance diagram is shown below AP 3 13



14. a Derive the expression for fault current in line to ground fault on an unloaded generator in terms of symmetrical components. AN 4 13

Or

- b Derive the expression for fault current in line to line fault on an unloaded generator in terms of symmetrical components. AN 4 13

15. a State the applications of equal area criterion as applicable to SMIB system. AN 5 13

Or

- b Derive the swing equation of a single machine connected to an infinite bus system. AN 5 13

PART – C (Marks 1*15 = 15)

<i>Q.No</i>	<i>Questions</i>	<i>BTL</i>	<i>CO</i>	<i>Marks</i>
-------------	------------------	------------	-----------	--------------


16. a With a neat flow chart describe the solution of swing equation by modified Euler method.

AN 5 15

Or

- b For the system shown determine the voltages at the end of first iteration by Gauss – Seidel method and also find the slack bus power. Assume base MVA as 100.

AP 2 15

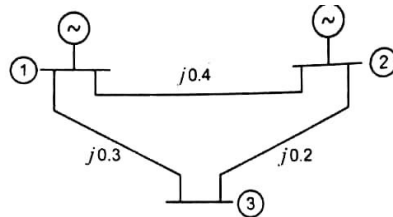

Bus No.	Voltage	Generator		Load		Q_{min}	Q_{max}
		P	Q	P	Q		
1	1.05	-	-	-	-	-	-
2	1.02p.u	0.3p.u	-	-	-	-10	100
3	-	-	-	0.4p.u	0.2p.u	-	-