

THE KAVERY ENGINEERING COLLEGE*(An Autonomous Institution)***UG/PG DEGREE END SEMESTER THEORY EXAMINATIONS APRIL/MAY 2026***Fifth Semester**Electronics and Communication Engineering***EC3551 – TRANSMISSION LINES AND RF SYSTEMS****(Smith Charts must be provided)***Regulations - 2021**Duration : 3 Hrs**Maximum : 100 Marks***PART – A (ANSWER ALL QUESTIONS) (Marks 10*2=20)**

<i>Q.No</i>	<i>Questions</i>	<i>BTL</i>	<i>CO</i>	<i>Marks</i>
1.	Sketch the equivalent circuit of a unit length of transmission line.	L2	1	2
2.	Distinguish phase distortion with frequency distortion.	L1	1	2
3.	State the relationship between standing wave ratio and magnitude of reflection co efficient.	L2	2	2
4.	Why is quarter wave line called an impedance inverter?	L1	2	2
5.	Write the equation to determine the position of the stub.	L1	3	2
6.	Calculate the standing wave ratio if the reflection co-efficient of a line is 0.3 $\angle -66^\circ$.	L2	3	2
7.	Infer the dominant modes of a rectangular waveguide.	L2	4	2
8.	State the features of TM mode.	L1	4	2
9.	Classify RF field effect transistors based on physical construction	L2	5	2
10.	Interpret the importance of voltage controlled oscillator in RF system.	L1	5	2

PART – B (ANSWER ALL QUESTIONS) (Marks 5*16 = 80)

<i>Q.No</i>	<i>Questions</i>	<i>BLT</i>	<i>CO</i>	<i>Marks</i>
11.	a i Derive the expression for open and short-circuited impedance.	L2	1	8
	ii Describe about the reflection on a line not terminated with its characteristic impedance.	L2	1	8
	Or			
	b i Draw and explain the reflection loss due to mismatch between source and load impedances.	L2	1	8
	ii Illustrate Z_0 and in terms of primary constants and explain the significance of Characteristic Impedance.	L2	1	8
12.	a i A 30m long lossless transmission line with $Z_0 = 50\Omega$ operating at 2 MHz is terminated with a load $Z_L = 60 + j40 \Omega$. If $u = 0.6c$ (c is velocity of light, u is phase velocity) on the line, Calculate (i) Reflection Coefficient, (ii) Standing wave ratio (iii) Input impedance.	L2	2	8
	ii Compute the transmitter end impedance of a HF line having characteristic impedance of 50Ω . The line is of length 1.185λ and is terminated in a load of $110 + j80 \Omega$.	L2	2	8

Or

	b i	Summarize the effect of the reflection losses on power delivered to the load on an unmatched line.	L2	2	8
	ii	Formulate the expression for maximum and minimum impedances on the lossless line.	L2	2	8
13.	a	For a 50Ω transmission line terminated with a $35+j35\Omega$ inductive load, determine the lengths of two parallel stubs and their respective positions using a Smith chart to achieve impedance matching. The stubs are separated by a distance of $\lambda/4$.	L3	3	16
Or					
	b	Design a single stub match for a load of $150+j225\Omega$ for a 75Ω line at 500 MHz using smith chart.	L3	3	16
14.	a	A rectangular air filled copper waveguide with dimension 0.9inch x 0.4inch cross section and 12 inch length is propagated at 9.2 GHz with a dominant mode. Calculate cutoff frequency, guide wavelength, phase velocity and characteristic impedance.	L3	4	16
Or					
	b	Calculate the cutoff wavelength, the guided wavelength and the characteristic wave impedance of a circular waveguide whose internal diameter is 4 cm for a 9 GHz signal propagated in the TE ₁₁ mode.	L3	4	16
15.	a	Examine the different operating modes of a bipolar junction transistor with appropriate diagram.	L4	5	16
Or					
	b	Analyze the performance impact of (i) Filters (ii) Couplers (iii) Power Amplifiers and (iv) Low Noise amplifiers in RF Design.	L4	5	16